2102440 Introduction to **Microprocessors**

Chapter 10 8253 Programmable Interval Timer/Counter Suree Pumrin, Ph.D.

Topics

- Interfacing with 8086/8088
- > Programming
- ≻ Mode

2102440 Introduction to Microprocessors

8253/54 Timer (I)

	4		-	~ .	L
0/	4	1		24	h Acc
D6	9	2		23	D WR
D5	d	3		22	RD
D4	0	4	8	21	CS
D3	d	5		20	D A1
D2	9	6	2	19	D AO
D1	9	7		18	CLK 2
D0	0	8	5	17	DOUT 2
CLK 0	D	9		16	GATE 2
OUT 0	0	10	3	15	CLK 1
GATE 0	0	11		14	GATE 1
GND	d	12		13	DOUT 1

• The 8253/54 Programmable interval timer is used to generate a lower frequency for various uses, e.g., the beep sound

CS	A1	A0	Port
0	0	0	Counter 0
0	0	1	Counter 1
0	1	0	Counter 2
0	1	1	Control register
1	x	x	8253/54 is not selected

8253/54 Timer (II)

Microprocessor		Counter
interface	no nin the	input/output
		CLK 0
(D7 - D0)		GATE
V V		
	0050	
	8253	GATE
m 1 12 65,236		
A0		CIK2
A1		GATE
is its own port.		
and to lease	0	
CS	ĭ	

- > There are three counters.
- > The input frequency can be divided from 1 to 65536.
- Input clock frequency is 0-2 MHz for 8253, up to 8 MHz for 8254, and up to 10 MHz for 8254-2.
- > Shape of the output frequency:
 - Square-wave
 - One-shot
 - Square-wave with various duty . cycles.
- > Gate is used to enable (High) or disable (Low) the counter.
- > Bidirectional bus D0-D7 is connected to D0-D7 of the system bus.

Architecture of the 8253/54



5

Control Word (I)

> D0

- Binary number divisor → 0000-FFFFH
 - Divisor = 65536 if the counter is loaded with 0 for both the low and the high bytes.
- BCD divisor → 0000-9999H
 - Divisor = 10000 if the counter is loaded with 0 for both the low and the high bytes.
- > D1, D2, and D3: Mode selection
 - Mode 0: Interrupt on terminal count
 - Mode 1: Programmable one-shot
 - Mode 2: Rate generator
 - Mode 3: Square wave rate generator
 - Mode 4: Software triggered strobe
 - Mode 5: Hardware triggered strobe

8253/54 Control Word Format



2102440 Introduction to Microprocessors

6

Control Word (II)

> D4 and D5 for RL0 and RL1

- RL0 and RL1 indicate the size of the divisor.
 - Read/write the least significant byte (LSB) only
 - Read/write the most significant byte (MSB) only
 - Read/write the LSB first then followed by the MSB
- We can write the value of the divisor into 8253/54 timer and read the contents of the counter at any time.
- D6 and D7 are used to select which of the three counters: counter 0 (00), counter 1 (01), and counter 2 (10).

Mode 0: Interrupt on terminal count



- It is used to generate an interrupt to the microprocessor after a certain interval of time.
- > The output is initially low after the mode is set. The output remains LOW after the count value is loaded in the counter.
- > The process of decrementing the counter continues till the terminal count is reached, i.e., the count become zero and the output goes HIGH. The output remains high until it reloads a new mode of operation or new count.
- The GATE signal is high for normal counting. When GATE goes low counting is terminated and the current count is latched till the GATE goes high again.

2102440 Introduction to Microprocessors

Mode 1: Programmable one-shot



- > The 8253/54 can be used as a monostable multivibrator.
- The gate input is used as trigger input in this mode. Normally, the output remains high until the count is loaded and a trigger is applied.
- The duration of the quasistable of the monostable multivibrator is decided by the count loaded in the count register. 2102440 Introduction to Microprocessors
 ¹⁰

Mode 2: Rate generator



- > Divide by N counter.
- > The output is normally high after initialization.
- > If N is loaded as the count value, after N pulses, the output becomes low for one clock cycle.
- Whenever the count becomes zero another low pulse is generated at the output.

11

9

Mode 3: Square wave rate generator



- > It is similar to mode 2.
- When, the count N loaded is EVEN, half of the count will be high and half of the count will be low.
- When, the count N loaded is ODD, the first clock pulse decrements it by 1. Then half of the remaining count will be high and half of the remaining count will be low.

Mode 4: Software triggered strobe



- After the mode is set, the output goes high. ≻
- The counter automatically begins to decrement (count down) one clock pulse after it is loaded with the initial value through software.
- When the GATE signal goes low the count is latched.
- On the terminal count, the output goes low for one clock cycle, and Þ then again goes high. This low pulse can be used as a strobe.

2102440 Introduction to Microprocessors

Mode 5: Hardware triggered strobe



- When the terminal count is reached, the output goes low for one clock cycle. ≻

2102440 Introduction to Microprocessors

Example 1

- \rightarrow Pin CS of a given 8253/54 is activated by binary address A7 - A2 = 100101
 - Find the port addresses assigned to this 8253/54. Counter $0 \rightarrow$ Port address = 1001 01 00 = 94H Counter 1 \rightarrow Port address = 1001 01 01 = 95H Counter 2 \rightarrow Port address = 1001 01 10 = 96H Control register → Port address = 1001 01 11 = 97H
 - Find the configuration for this 8253/54 if the control register is programmed as follows. MOV AL. 00110110
 - OUT 97H. AL
 - $D7-D6 = 00 \rightarrow select counter 0$
 - D5-D4 = 11 \rightarrow the low byte read/write is followed by the high byte.
 - $D3-D1 = 011 \rightarrow$ select mode 3 (square wave)
 - $D0 = 0 \rightarrow$ select the binary counting

Example 2

- > Use the port addresses in Ex. 1 to program counter 2 for binary count of mode 3 (square wave) to divide CLK2 by number C26AH and find the frequency of OUT2 if CLK2 = 1.8 MHz.
 - The control word = 10110110

MOV AL, B6H	; counter 2, mode 3, binary
OUT 97H, AL	; send it to control register
MOV AX,C26AH	; load the divisor
OUT 96H, AL	; send the low byte to counter 2
MOV AL, AH	
OUT 96H, AL	; send the high byte to counter 2

- ovte to counter 2
- The output frequency for OUT2 = 1.8 MHz is divided by C26AH (49770 D). OUT 2 frequency is a square wave of 36 Hz.

13

Example 3

Using the port address in Ex.1, show the programming of counter 1 to divide CLK1 by 10,000, producing the mode 3 square wave. Use the BCD option in the control byte.

MOV AL, 77H	; counter 1, mode 3, BCD
OUT 97H, AL	; send it to control register
SUB AL, AL	; AL = 0 load the divisor for 10,000
OUT 95H, AL	; send the low byte
OUT 95H, AL	; send the high byte

2102440 Introduction to Microprocessors

17

8253 Chip Connections in the PC

